

Problem 1.4

Consider the circuit of Fig. P1.4.

- (a) Determine v_{out} and node voltage V_x .
- (b) What is the apparent circuit function?
- (c) What circuit modifications (if any) lead to a better design?

mark
diagram

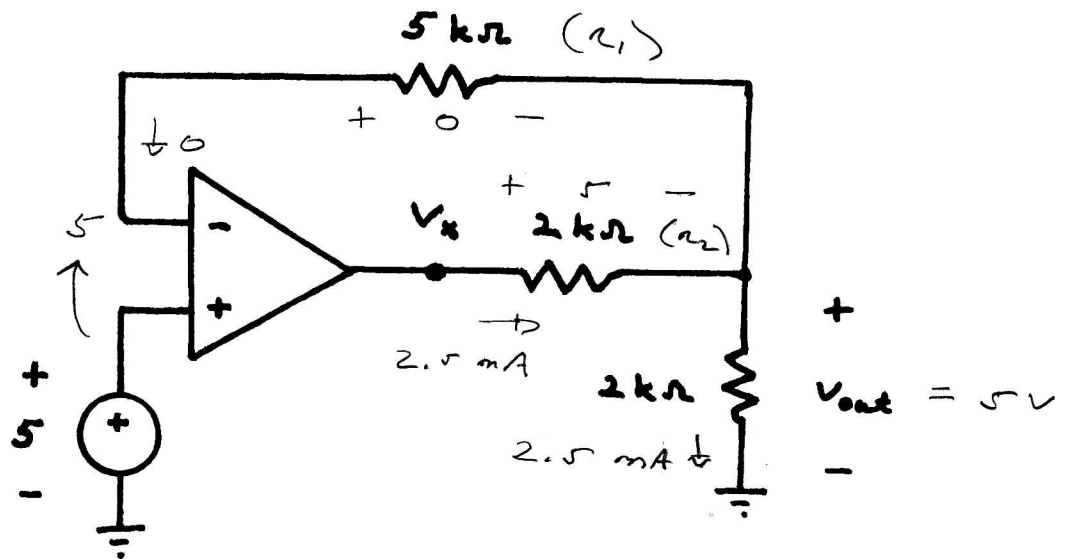


Figure P1.4

$$V_x = 5 + 5 = 10$$

- b) unity-gain buffer, $v_{out} = v_{in}$
no current drawn from input source
- c) Eliminate r_1 and $r_2 \rightarrow$ shorts

Problem 1.8

mark
diagram

Determine node voltages V_a and V_b in the circuit of Fig. P1.8.

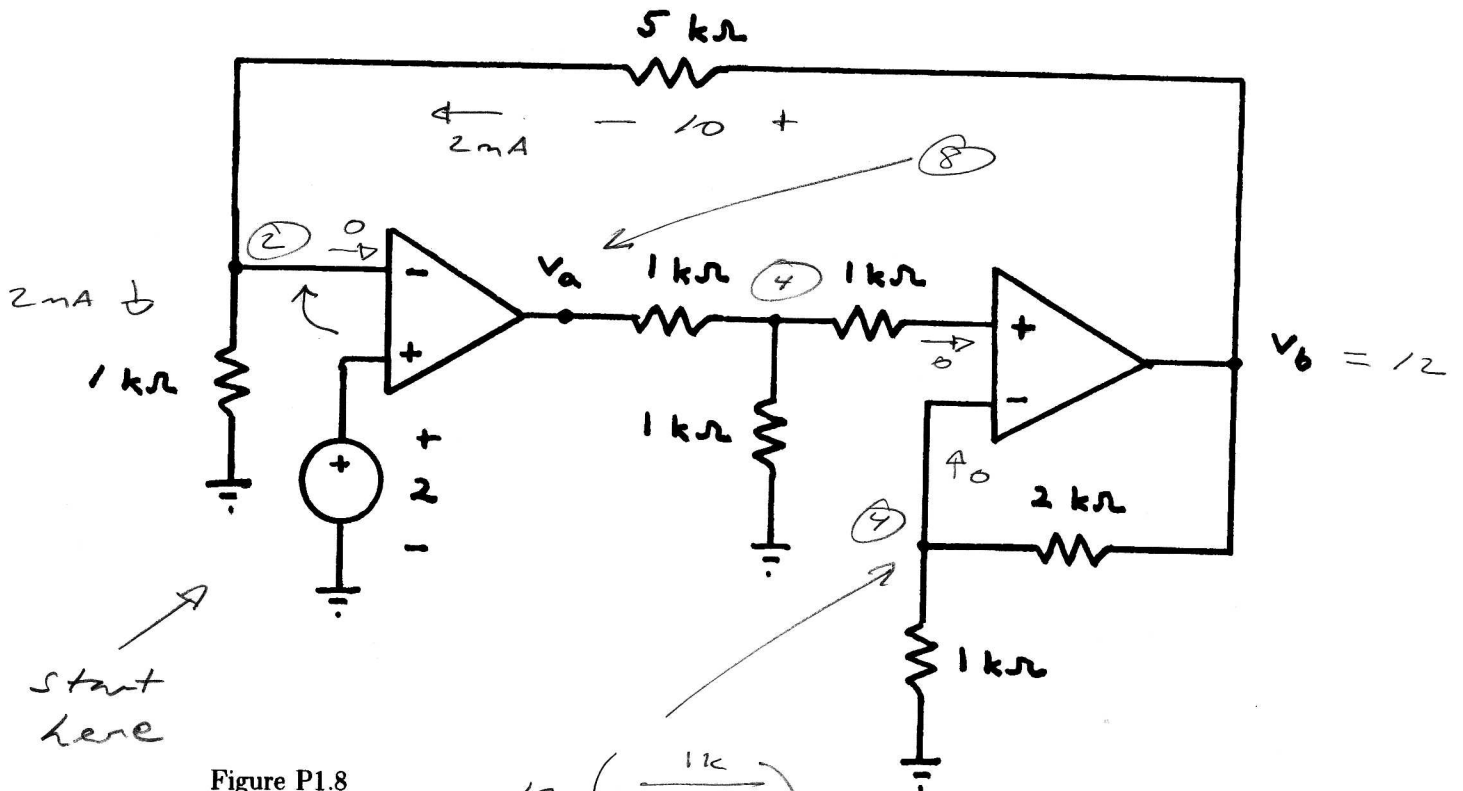


Figure P1.8

$$12 \left(\frac{1k}{1k + 2k} \right) = 4$$

non-inverting
amplifier

$$\text{gain} = \left(1 + \frac{2k}{1k} \right) = 3$$

c.) continued

$$i_{out}(n+n_3) = a i_{out} n - b v_1$$

$$i_{out} = \frac{-b v_1}{(1-a)n + n_3}$$

no R dependence
(current source)
if $a = 1$

Problem 1.20

Consider the circuit of Fig. P1.20.

- (a) Determine node voltages v_a and v_b in terms of node voltage v_x .
- (b) Determine voltage v' and the output current i_{out} .
- (c) Show the separate consequences of mismatched R_1 and R_2 resistors.

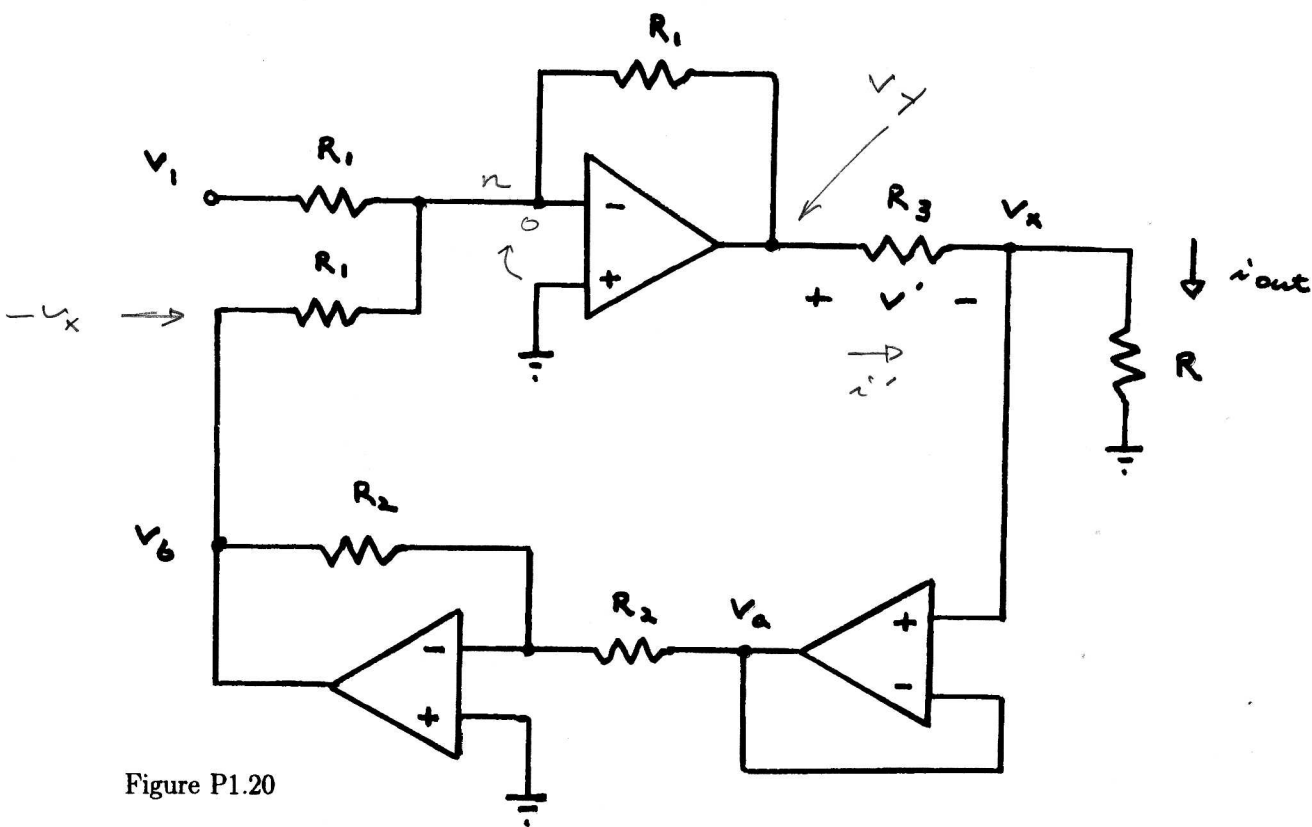


Figure P1.20

a)

$$v_b = -v_a = -v_x \quad v_a = v_x$$

b)

At node n , $\frac{v_1}{R_1} + \frac{-v_x}{R_1} + \frac{v_y}{R_1} = 0 \rightarrow v_y = v_x - v_1$

$$v' = v_y - v_x = -v_1 \rightarrow i' = i_{out} = \frac{-v_1}{R_3}$$

(voltage controlled current source)

c)

R_1 or R_2 mismatch $\rightarrow v_y = a v_x - b v_1$

$$a \neq 1, b \neq 1$$

see top
↑