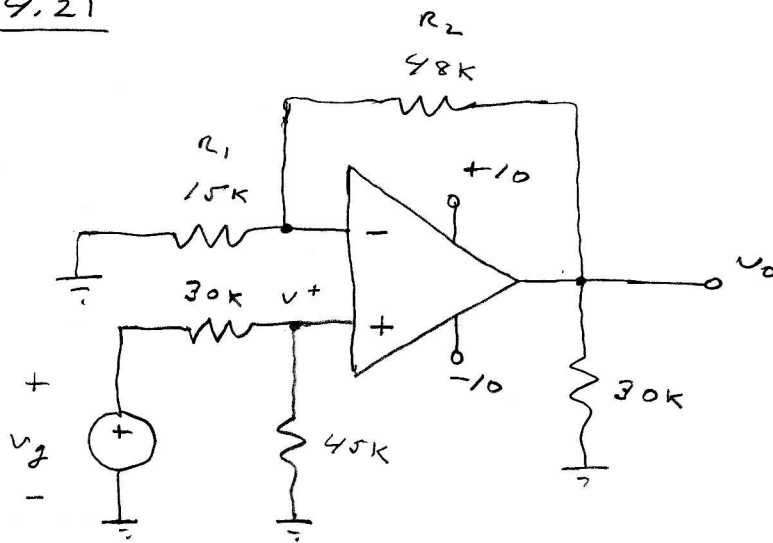


4.21



$$a) \quad v^+ = v_g \left( \frac{45k}{45k + 30k} \right) = \frac{3}{5} v_g$$

$$\text{But } v_o = v^+ \left( 1 + \frac{R_2}{R_1} \right)$$

(recall the non-inverting amplifier)

$$\rightarrow v_o = \left( 1 + \frac{48k}{15k} \right) \left( \frac{3}{5} \right) v_g = 2.52 v_g$$

$$\text{so if } v_g = 3V, \quad v_o = 7.56V$$

$$b) \quad \text{For linear mode, } -10 \leq v_o \leq +10$$

$$\rightarrow v_g \leq \frac{10}{2.52} = 3.97$$

$$\rightarrow v_g \geq \frac{-10}{2.52} = -3.97$$

$$c) \quad v_g = 5V, \quad 48k \rightarrow R_2$$


$$v_o = \frac{3}{5} (5) \left( 1 + \frac{R_2}{15} \right) < 10$$

$$\left( 1 + \frac{R_2}{15} \right) < \frac{10}{3}$$

$$\frac{R_2}{15} < \frac{7}{3}$$

$$\rightarrow R_2 < 35k$$

4.28

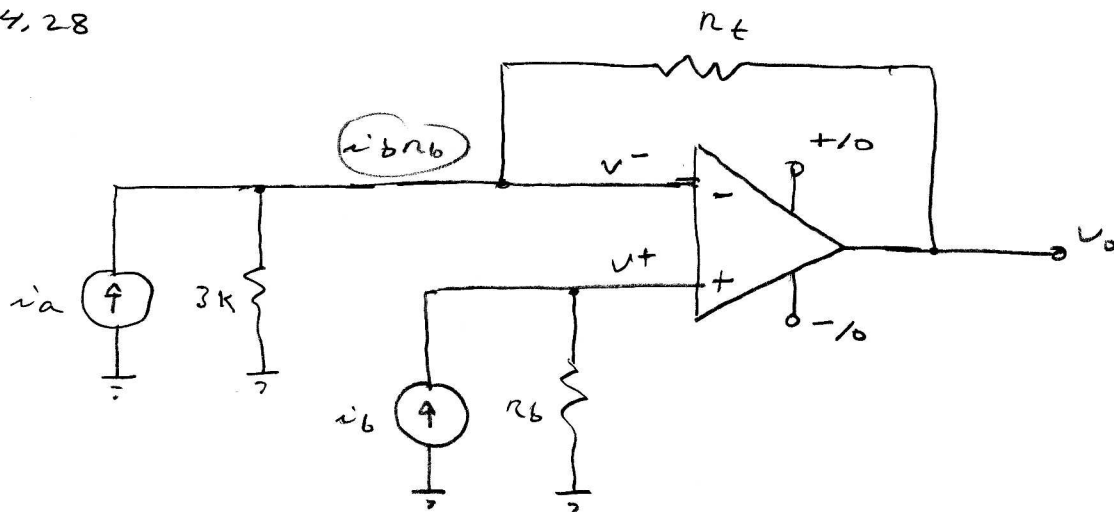

$$\text{Want } v_o = 2000 (i_b - i_a)$$

↑  
 $\Omega$

$$v^+ = i_b r_b = v^-$$

so at the  $v^-$  node,

$$i_a - \frac{i_b r_b}{3} + \frac{v_o - i_b r_b}{R_t} = 0 \quad (\text{KCL})$$

$$\rightarrow v_o = R_t \left\{ \frac{r_b}{R_t} \left( 1 + \frac{R_t}{3} \right) i_b - i_a \right\}$$


$$R_t = 2k \quad (2000 \Omega)$$

$$\frac{r_b}{R_t} \left( 1 + \frac{R_t}{3} \right) = \frac{r_b}{2} \left( 1 + \frac{2}{3} \right) = 1$$

$$\rightarrow r_b = 1.2k$$

4.31

mark up  
diagram

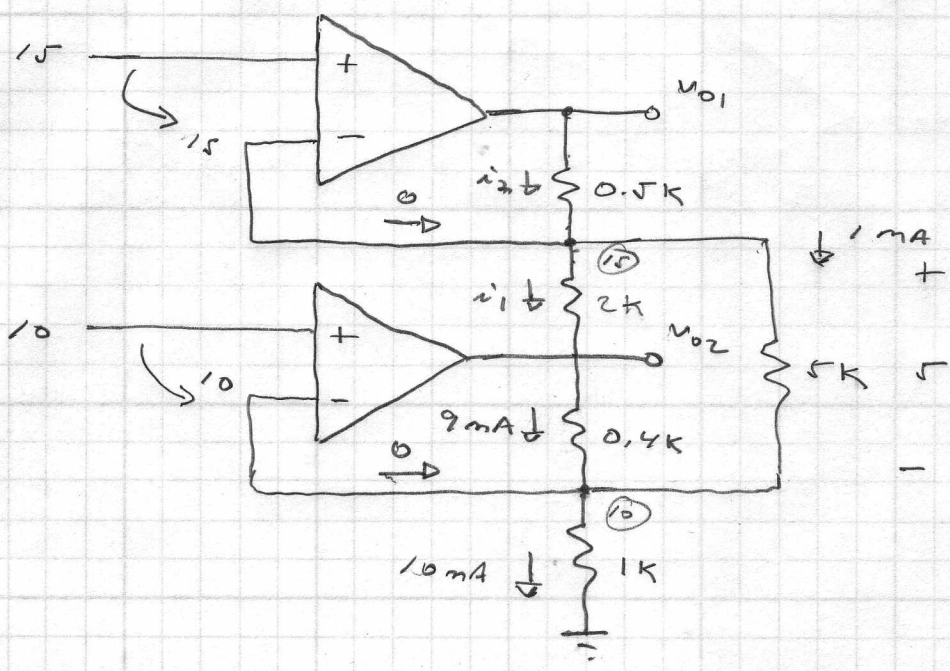

$$V_{02} = 10 + 9(0.4) = 13.6 \text{ V}$$

$$i_1 = \frac{15 - 13.6}{2} = 0.7 \text{ mA}$$

$$i_2 = 1 \text{ mA} + 0.7 \text{ mA} = 1.7 \text{ mA}$$

$$V_{01} = 15 + 1.7(0.5) = 15.85 \text{ V}$$