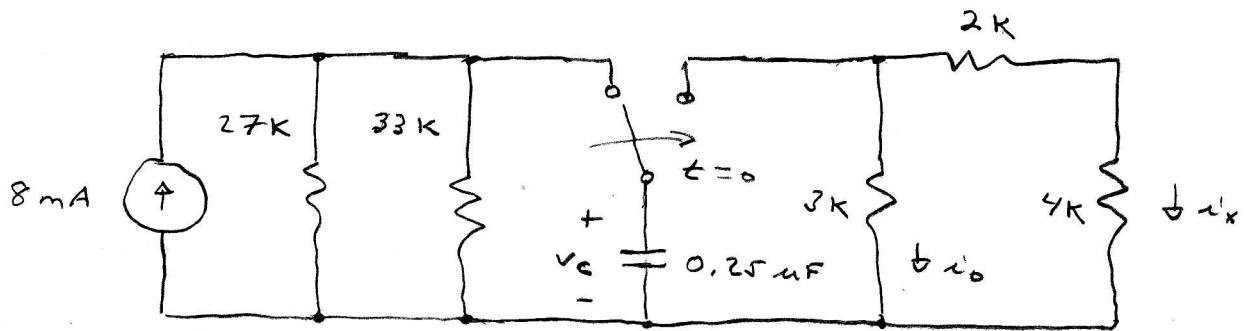


5.59

$$a) i_o(t) = i_o(\infty) + [i_o(0^+) - i_o(\infty)] e^{-\frac{t}{\tau}}$$

$$\tau = 0.25 \mu\text{F} \times \underbrace{3\text{k} \parallel (2\text{k} + 4\text{k})}_{2\text{k}} = 0.5 \text{ ms}$$

$$i_o(\infty) = 0 \quad (\text{capacitor discharged})$$

$$V_c(0^-) = 8 \text{ mA} \times 27\text{k} \parallel 33\text{k} = 118.8 \text{ V}$$

$$V_c(0^+) = V_c(0^-) \quad (\text{capacitor voltage continuous})$$

$$i_o(0^+) = \frac{118.8 \text{ V}}{3\text{k}} = 39.6 \text{ mA}$$

$$\rightarrow i_o(t) = (39.6 \text{ mA}) e^{-\frac{t}{0.5 \text{ ms}}}$$

$$b) i_x(t) = (19.8 \text{ mA}) e^{-\frac{t}{0.5 \text{ ms}}}$$

$$P_x(t) = i_x^2(4\text{k}) = 1.568 e^{-\frac{t}{0.5 \text{ ms}}} \text{ watts}$$

4-k resistor power dissipated

Let E_x = energy lost after 0.25 ms

$$E_x = \int_0^{0.25 \text{ ms}} 1.568 e^{\frac{-t}{0.5 \text{ ms}}} dt \quad (\text{joules})$$

$$= \left[-1.568 \times 0.5 \times 10^{-3} e^{\frac{-t}{0.5 \text{ ms}}} \right]_0^{0.25 \text{ ms}}$$

$$= 0.784 \left(1 - e^{-\frac{1}{2}} \right) \text{ mJ}$$

$$= 0.308 \text{ mJ}$$

Let E_s = initial stored energy

$$E_s = \frac{1}{2} (0.25 \mu\text{F}) \times (118.8)^2 \text{ V}^2$$

$$= 1.764 \text{ mJ}$$

$$\% \text{ dissipation} = \frac{0.308}{1.764} \times 100 = \underline{\underline{17.5}}$$