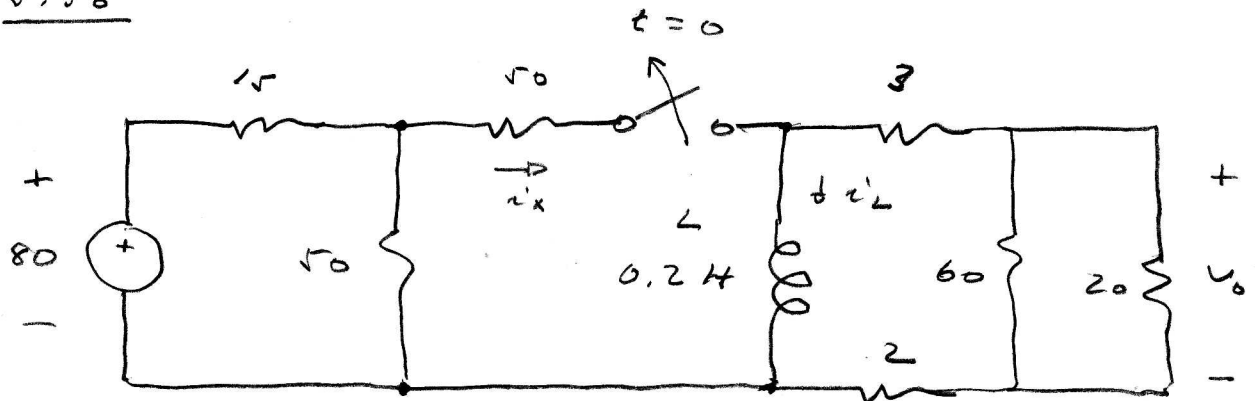



5.36

$$v_o(t) = v_o(\infty) + [v_o(0^+) - v_o(\infty)] e^{-\frac{t}{\tau}}$$

$$\tau = 0.2 \text{ H} / \underbrace{[3 + 60 // 20 + 2]}_{20 \Omega} = 10 \text{ ms}$$

$$v_o(\infty) = 0 \quad (\text{dead circuit})$$

At $t = 0^-$ $L \rightarrow$ short

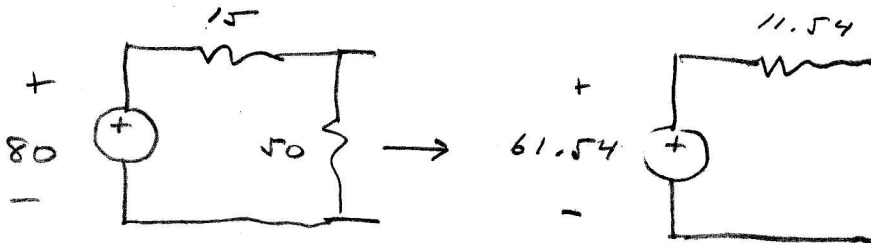


$$i_x(0^-) = i_L(0^-) = \frac{61.54}{11.54 + 50} = 1 \text{ A}$$

$$i_L(0^+) = i_L(0^-) = 1 \text{ A}$$

$$v_o(0^+) = -1 \text{ A} \times 15 \Omega = -15 \text{ V}$$


$$\rightarrow v_o(t) = (-15 \text{ V}) e^{-\frac{t}{10 \text{ ms}}}$$

5. 43

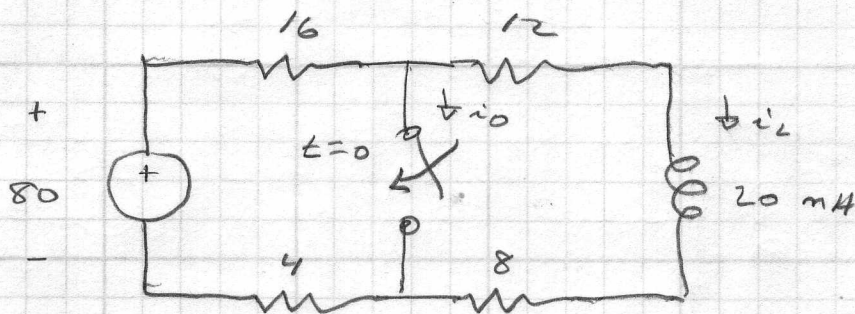

a) At $t = 0^-$, $i_L = \frac{80}{16 + 12 + 8 + 4} = 2A$
 $L \rightarrow$ short

$i_L(0^+) = 2A$

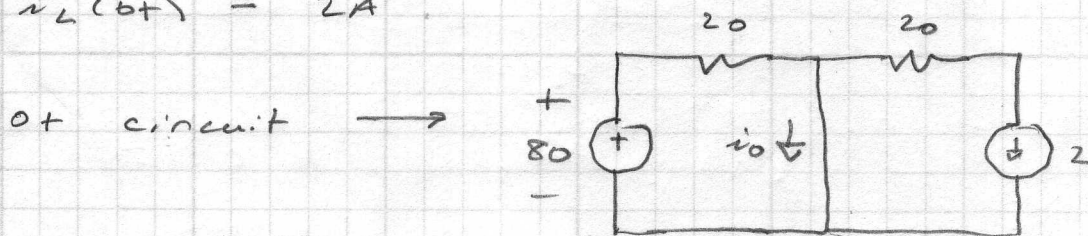

$i_o(0^+) = \frac{80}{20} - 2 = 2A$

$i_o(\infty) = \frac{80}{20} = 4A$

b) $i_o(t) = i_o(\infty) + [i_o(0^+) - i_o(\infty)] e^{-\frac{t}{\tau}}$

$\tau = \frac{20 \text{ mH}}{20 \Omega} = 1 \text{ ms}$

$i_o(t) = 4 + 2 e^{-\frac{t}{1 \text{ ms}}}$

c) $t : i_o = 2.8 A ? \rightarrow 2 e^{-\frac{t}{1 \text{ ms}}} = 0.2$

$t = 10 \text{ ms} \times \ln 10 = 23 \text{ ms}$