

Static Random Access Memories (SRAM)

Birdy Amrutur
amrutur@hpl.hp.com

Key features of SRAMs

Holds data statically:

As long as power is supplied to the chip, the data remains.

Data randomly accessible:

ReadData = Memory[Address]

Memory[Address] = WriteData

SRAMs Used as:

Embedded memory, e.g.:

First and second level caches in processors

Data buffers in various DSP chips

Standalone SRAMs:

Caches in computer systems

Main memory in low power applications


Typical sizes:

Embedded: upto 1Mbit


Standalone: upto 16Mbit

The system level view of SRAMs


Asynchronous interface

 


Used for stand alone SRAM chips

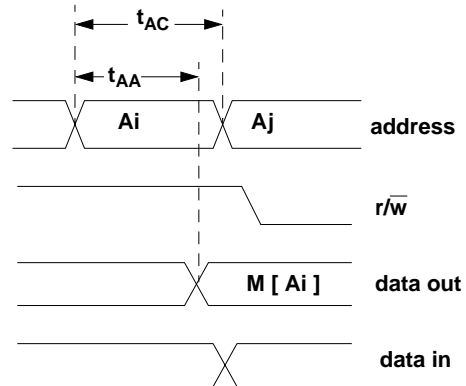


Synchronous interface

 


Used for embedded and standalone SRAMs

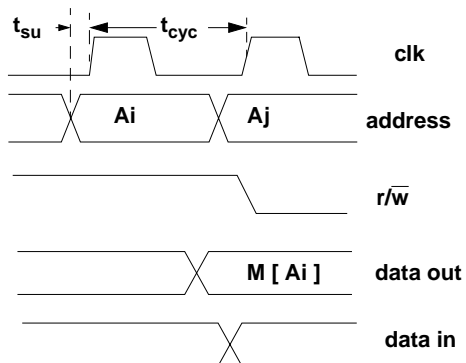


SRAM Architecture

 


CMOS SRAM cell

 


a) Static cell

 

b) 6T CMOS cell

 


c) 4T poly-R cell

 


d) 6T poly-PMOS cell


Reading a cell

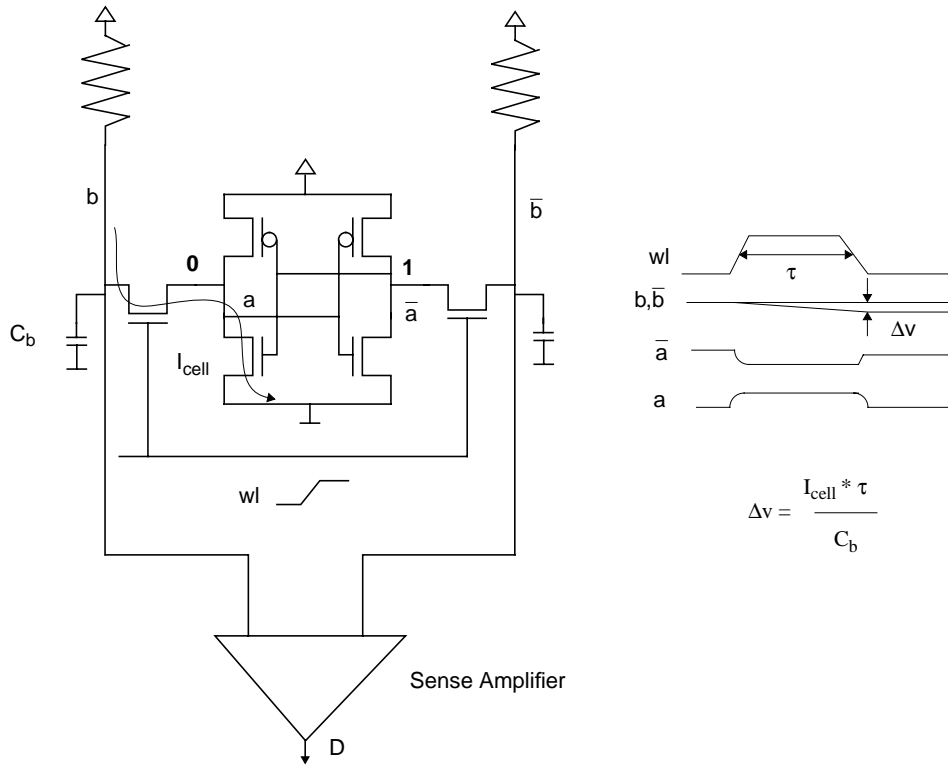

Writing a cell

 


Bitline precharge and load

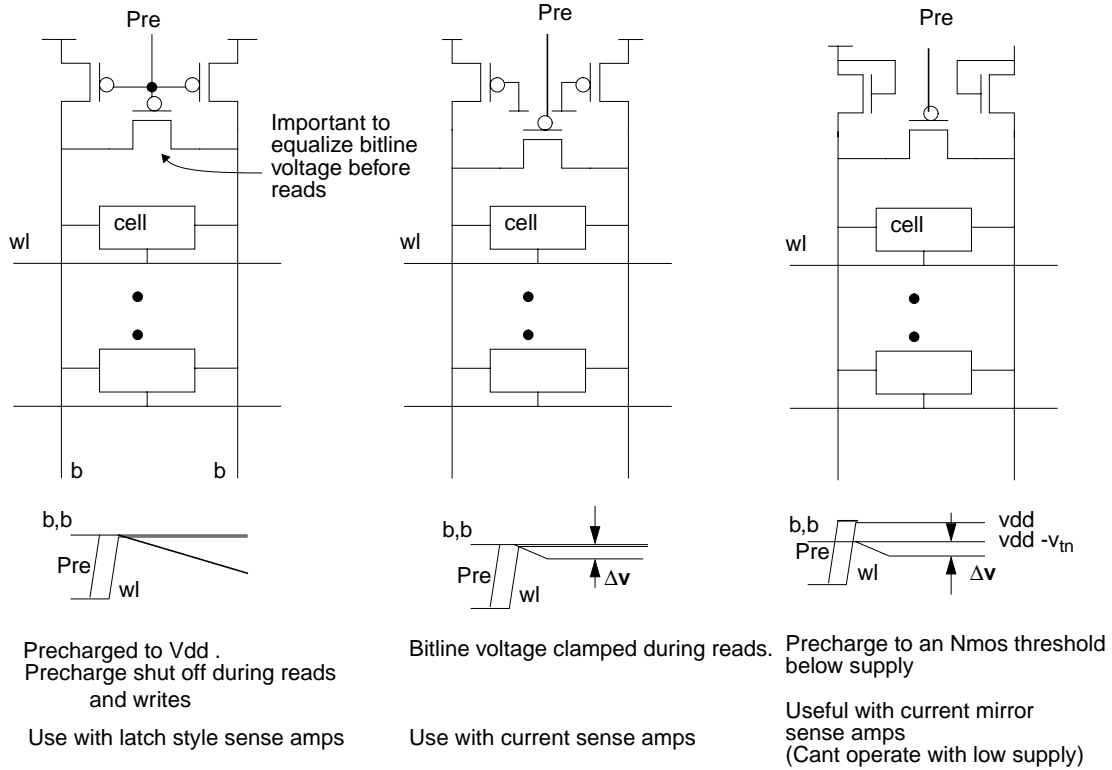


Sense amplifiers

 Need to amplify input bitline swing of ~100mV to full digital levels.




Current mirror amplifier

 

Latch type amplifier


Decoders

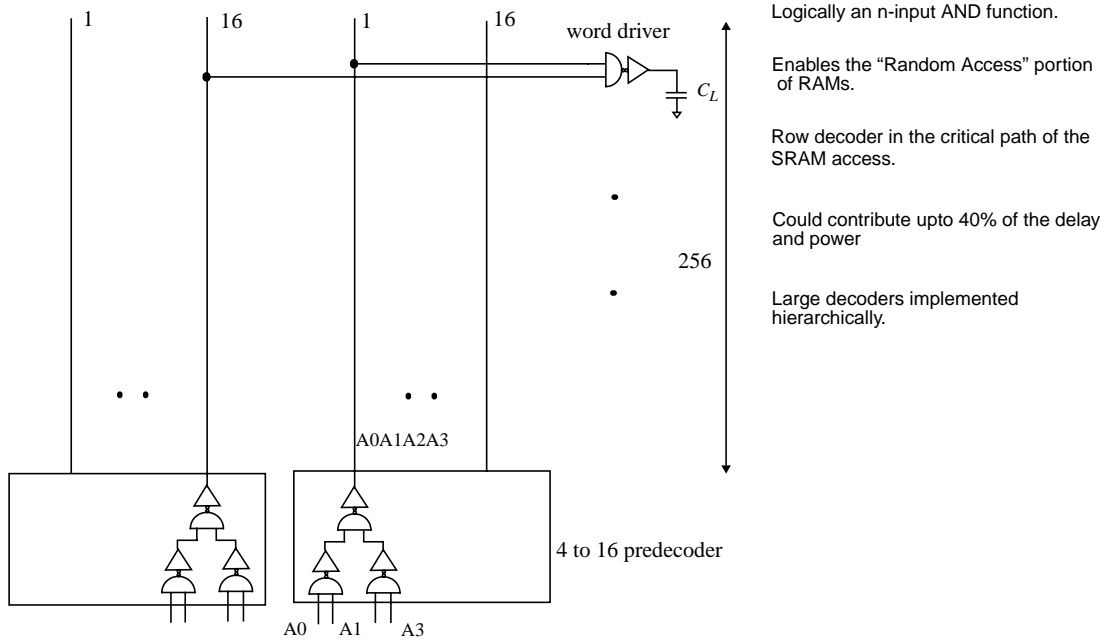

An 8 to 256 decoder


Sram Partitioning

Divided word line Architecture

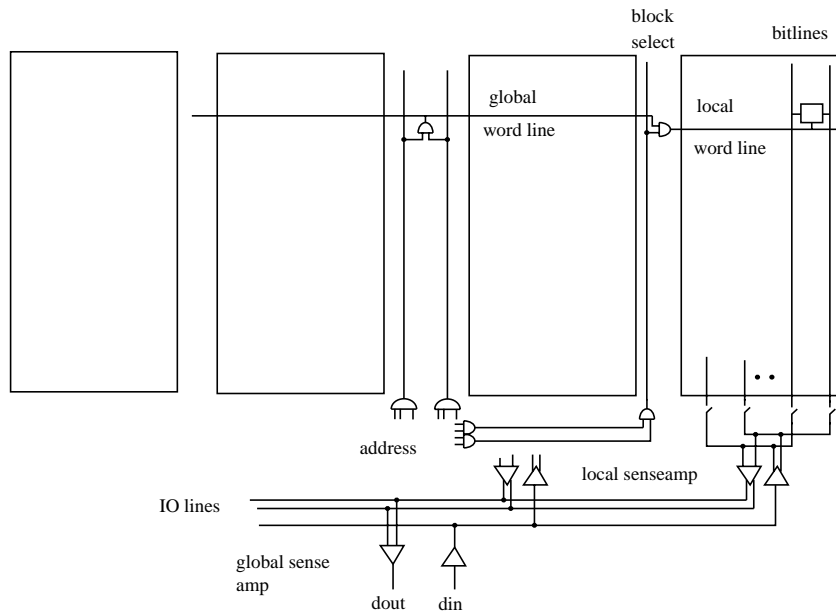

Use higher level metal for global word lines

Bitline partitioning

 

Use higher level metal for global bitlines


Partitioning summary

Partitioning involves a trade off between area, power and speed

For high speed designs, use short blocks(e.g 64 rows x 128 columns)
 Keep local bitline heights small

For low power designs use tall narrow blocks (e.g 256 rows x 64 columns)
 Keep the number of columns same as the access width to minimize wasted power



CMOS SRAM cell design-1

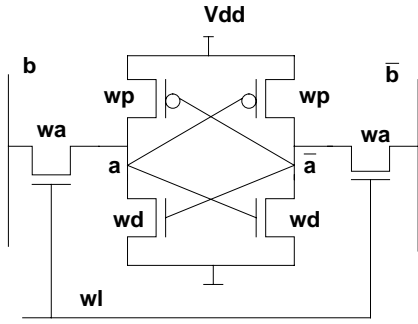

- Problem: Find wa, wd, wp such that
- 1) minimize cell area
 - 2) obtain good read and write cell margins
 - 3) good soft error immunity
 - 4) good cell read current


in that order

Conflicting goals!

  

CMOS SRAM cell design-2

Read Stability

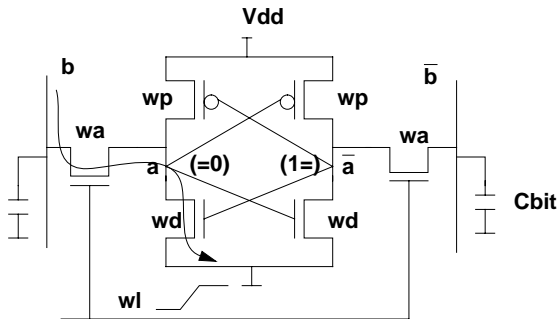



Usually Cbit is very big compared to internal node capacitances

Cell will flip if the "0" node bounces high enough to cause the "1" node to discharge

Simulate for worst case scenario with threshold and size mismatches in the cell which aids in flipping


To obtain good stability :
  
$$\beta = \frac{wd * (Vdd - Vtn)^2}{wa * (Vdd - Vtn)^2} = \frac{wd}{wa} > 2.5$$



CMOS SRAM cell design-3

Write Stability

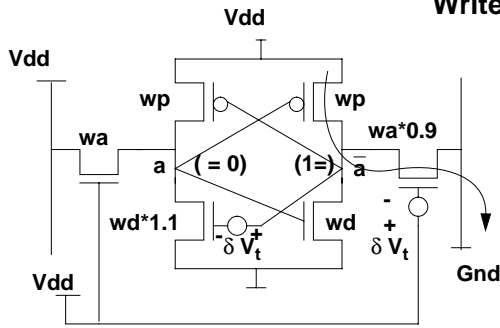


Cell is written by discharging the "1" node low. This causes the "0" node to charge up.

Need to ensure that

$$wa * \mu_n * (V_{dd} - V_{tn})^2 > wp * \mu_p * (V_{dd} - V_{tp})^2$$

 
Hence use minimum sized pMOS load devices.



Dynamic write noise margin

CMOS SRAM cell design-4

Soft Error Immunity

 


α -particle can create electron-hole pairs in the channel of a "off" transistor.

This causes the "off" transistor to leak away some of the stored charge.

Two solutions to the problem:

Increase stored charge ($> 20fC$) - use larger transistors (more capacitance), bigger voltages

 Use system level solution like redundancy bits for error detection and correction



Cell Layout

Simple layout in MOSIS design rule. Cell area is $66.5 \mu m^2$ ($1064\lambda^2$) in $0.5\mu m$ CMOS

Advanced processes with tighter rules + clever non-manhattan (non-right angle) layouts reduce cell area significantly (typically $\sim 650\lambda^2$)

Poly-R and poly-PMOS cells have 2-3 times smaller area as the load devices can be laid out on top of the nMOS transistors