
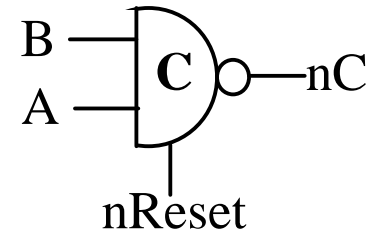


EE 577b – Fall 2001


Prof. Peter Beerel

Tips on homework 3



C-element

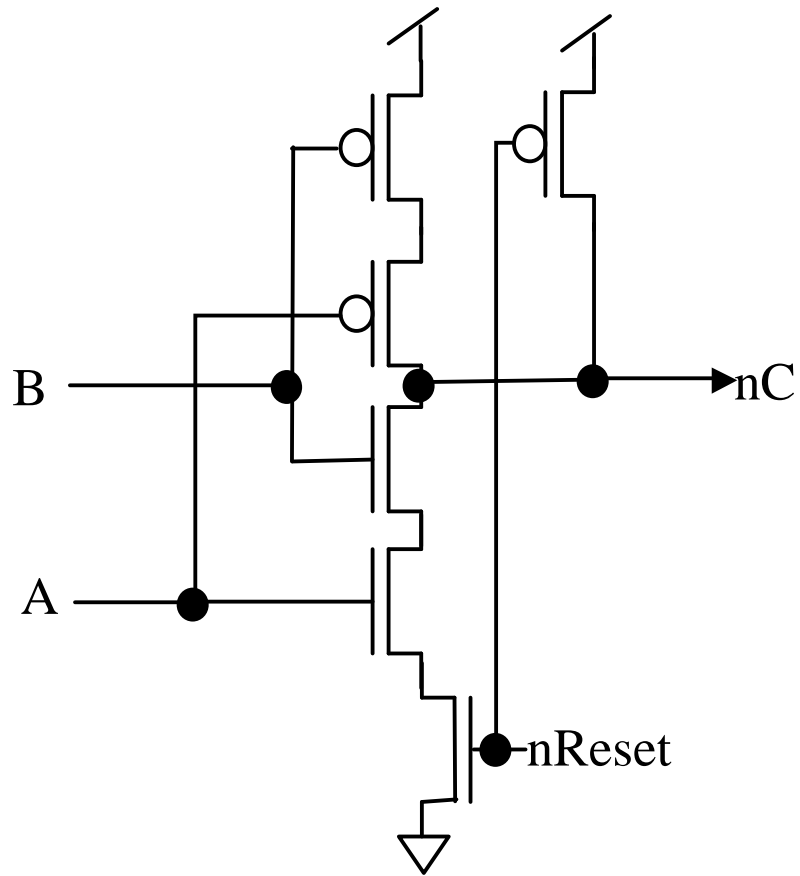


Staticizer

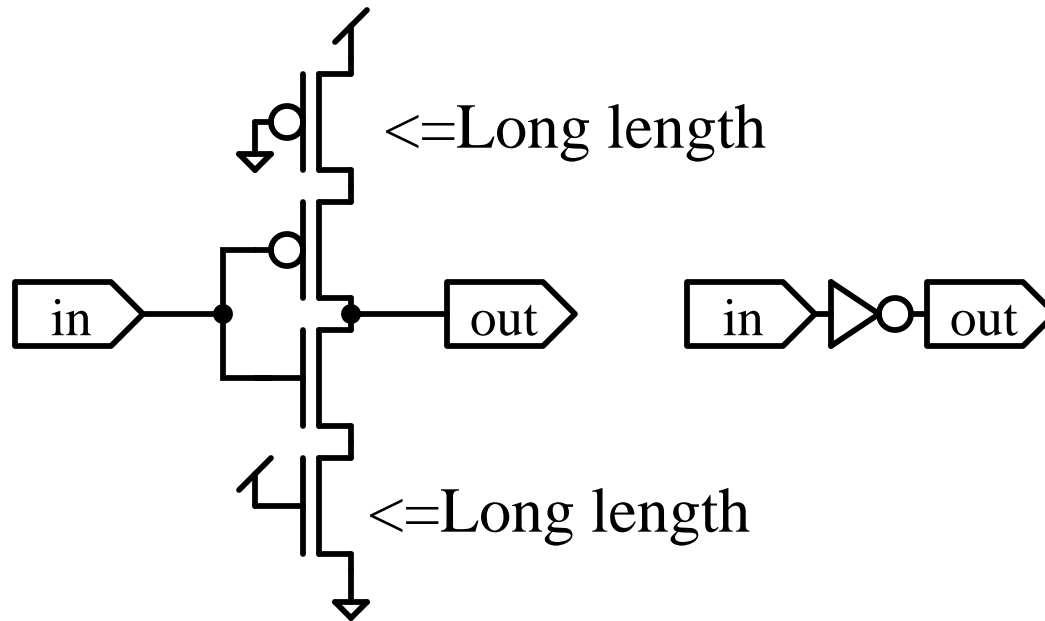


Weak condition half-buffer

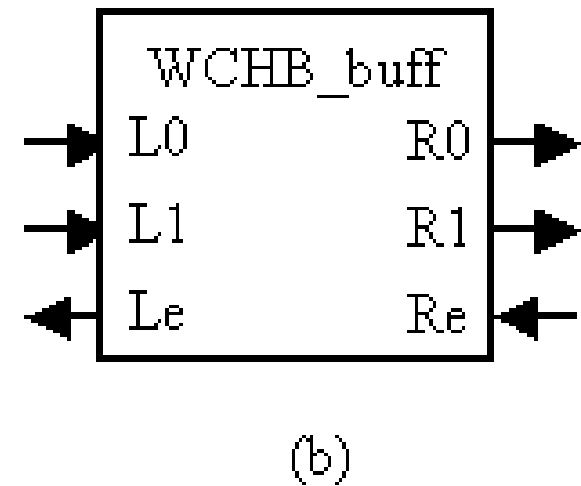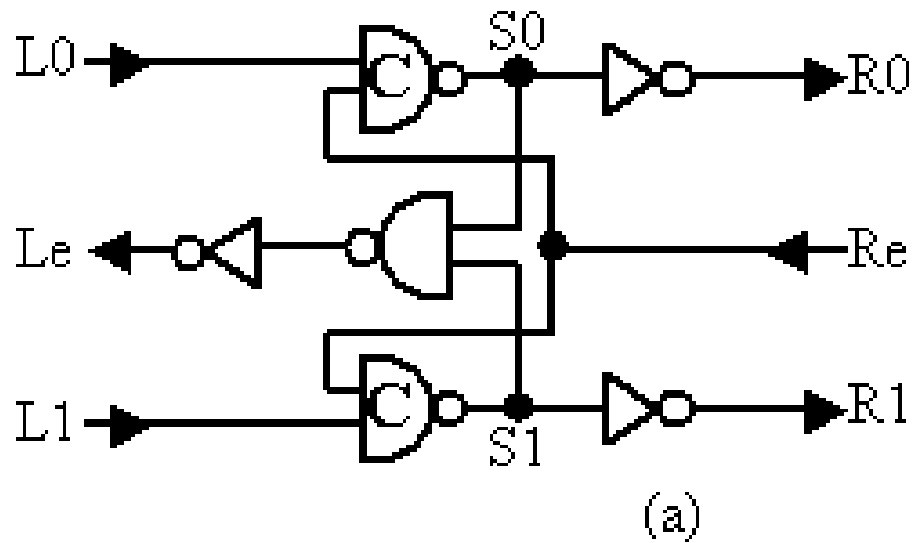


Bit Generator

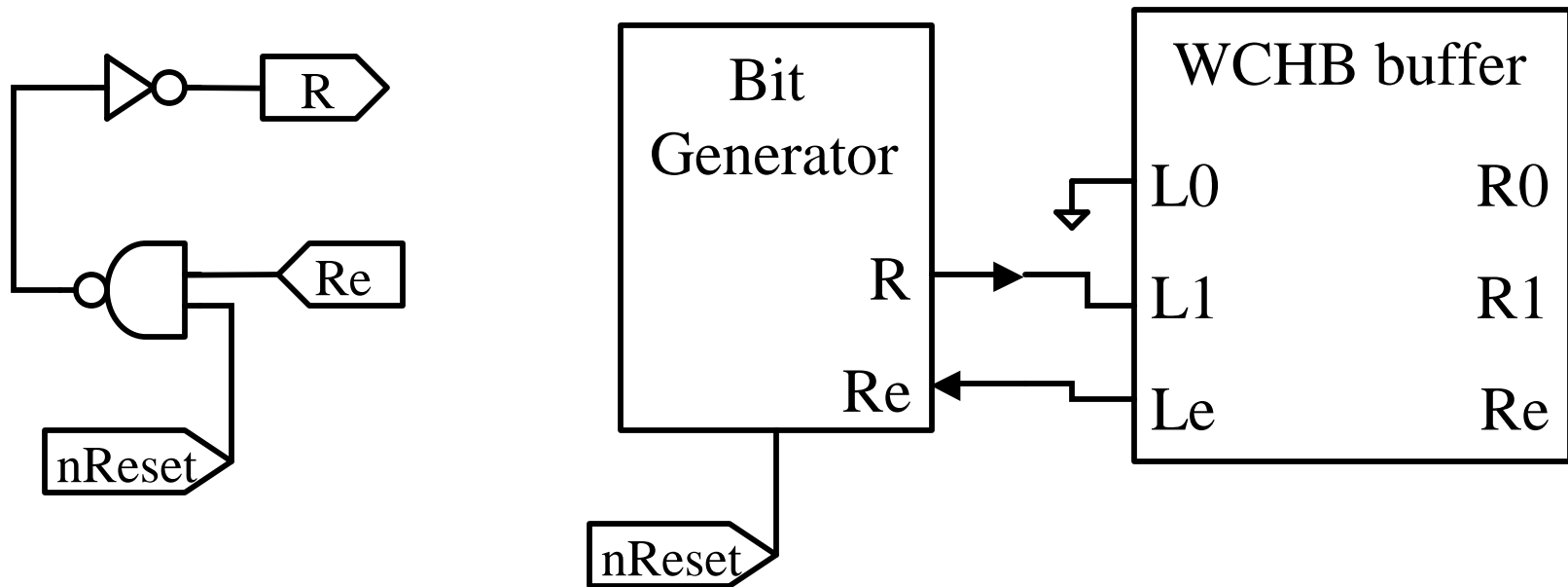



Bit Bucket

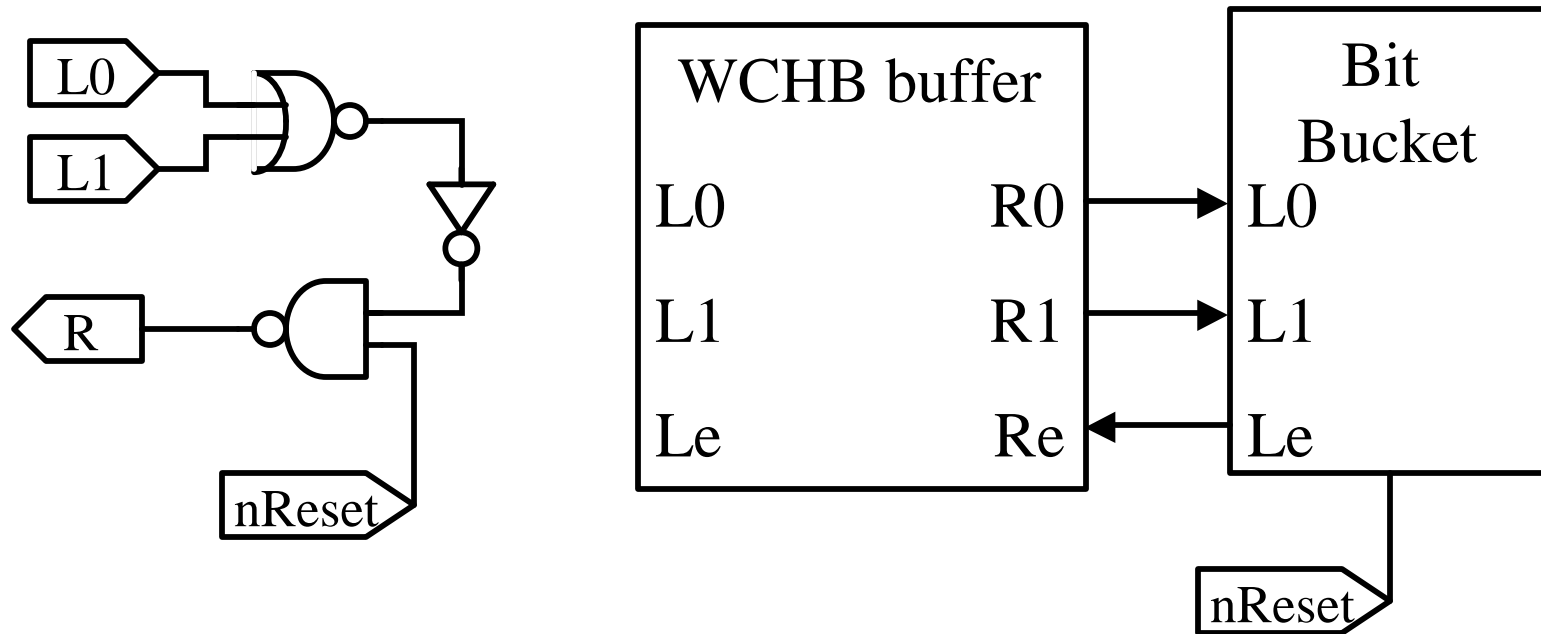


40 WCHB Buffers

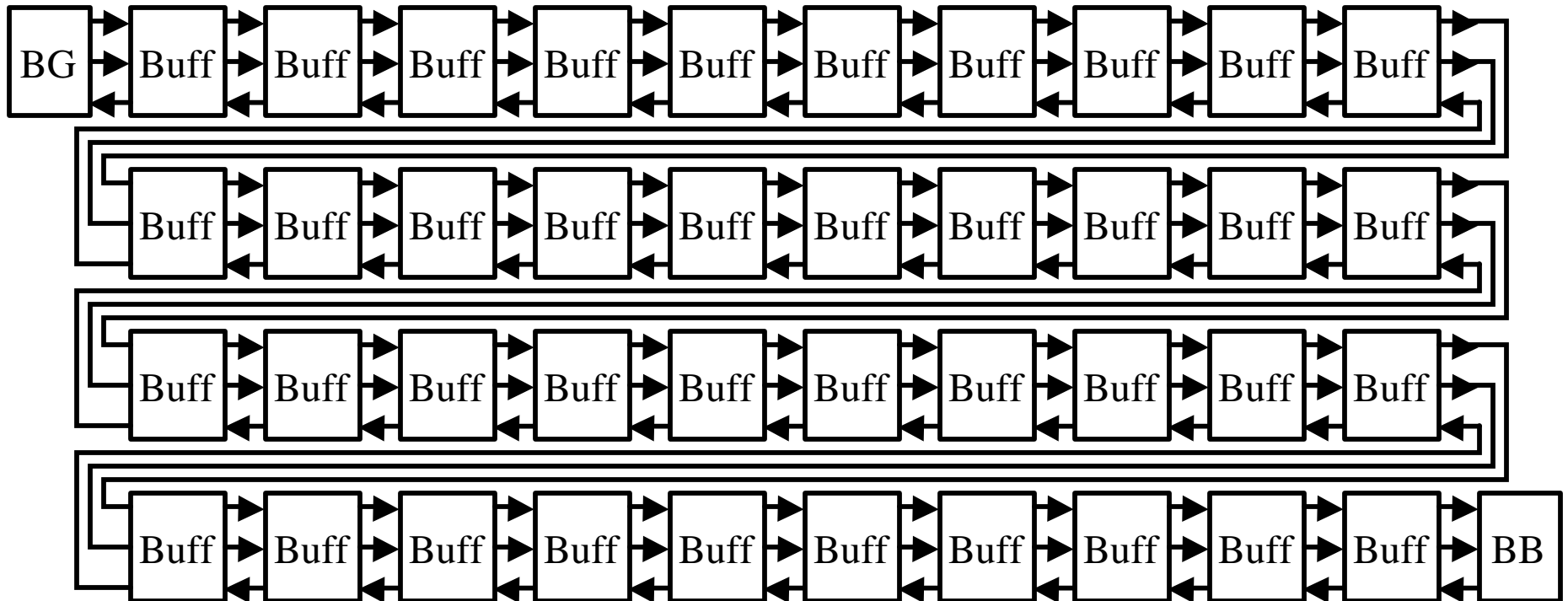

Pre-Charge Half-Buffer Full-Adder

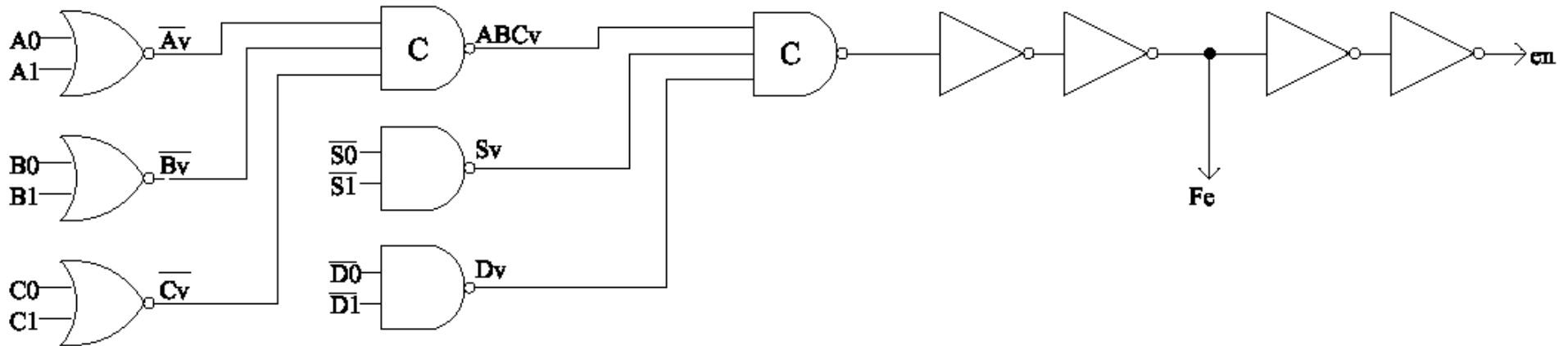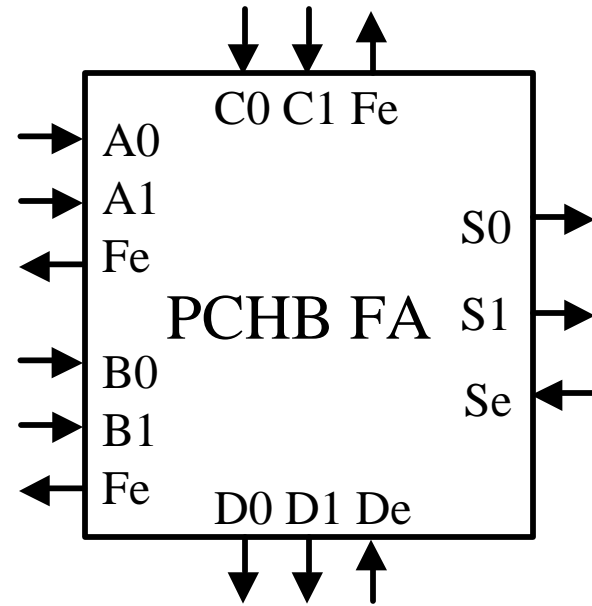

Pre-Charge Half-Buffer Full-Adder

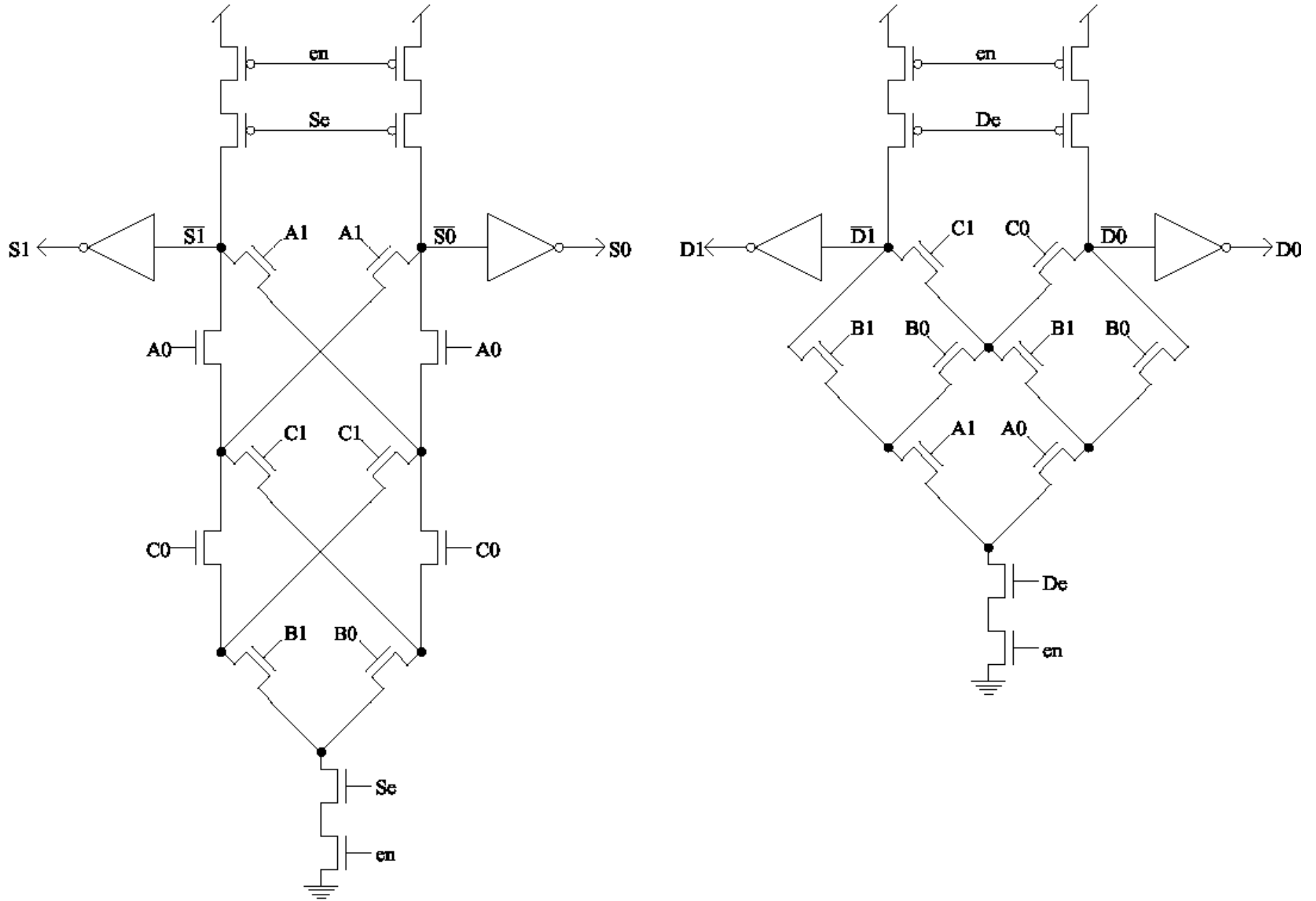

8 bit Ripple Carry PCHB Full-Adder

